
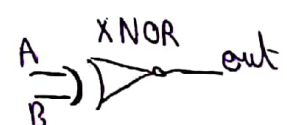
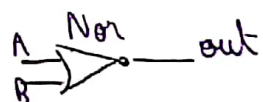
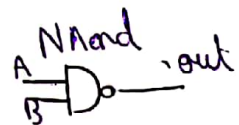
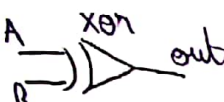


Logique Booléenne

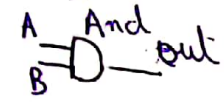

Not

A	S = \bar{A}
0	1
1	0

And

A	B	S = A . B
0	0	0
0	1	0
1	0	0
1	1	1

Or

A	B	S = A + B
0	0	0
0	1	1
1	0	1
1	1	1

Xor

A	B	S = A \oplus B
0	0	0
0	1	1
1	0	1
1	1	0

NAnd

A	B	S = $\overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

Nor

A	B	S = $\overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0

XNor

A	B	S = $\overline{A \oplus B}$
0	0	1
0	1	0
1	0	0
1	1	1

Associativité :

$$(A + B) + C = A + (B + C)$$

$$A \cdot (B \cdot C) = (A \cdot B) \cdot C$$

Distributivité :

$$A(B + C) = AB + AC$$

Theorème de Boole :

$$\left. \begin{array}{l} A + 1 = 1 \\ A \cdot 0 = 0 \\ A \cdot 1 = A \\ A + 0 = A \end{array} \right\} \begin{array}{l} A + A = A \\ A \cdot A = A \\ A + \bar{A} = 1 \\ A \cdot \bar{A} = 0 \end{array} \quad \bar{\bar{A}} = A$$

Loi de Morgan

$$\overline{A + B} = \bar{A} \cdot \bar{B}$$

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

$$\overline{A \oplus B} = \overline{AB + \bar{A}\bar{B}} = \overline{AB} \cdot \overline{\bar{A}\bar{B}}$$

$$= (\bar{A} + \bar{B}) \cdot (A + B)$$

$$= (A + \bar{B}) \cdot (\bar{A} + B) = \underbrace{A\bar{A}}_0 + AB + \bar{A}\bar{B} + \underbrace{B\bar{B}}_0$$

$$= AB + \bar{A}\bar{B}$$


A	B	C	S
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

$$\begin{aligned} S &= \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}C + ABC \\ &= \bar{A}C(\bar{B} + B) + A(\bar{B}C + BC) \\ &= \bar{A}C + A(B \oplus C) \end{aligned}$$


AB	00	01	11	10
0	0	0	1	0
1	1	1	0	1

$$S = AB\bar{C} + \bar{A}C + \bar{B}C$$

Exercice 1:

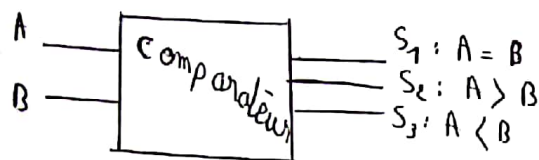

1)

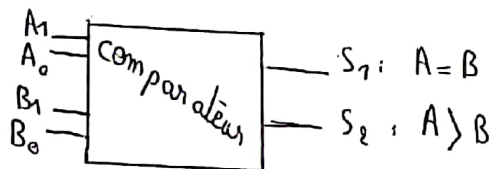

2)

A		B		S ₁ : A=B	S ₂ : A>B
A ₁	A ₀	B ₁	B ₀		
0	0	0	0	1	0
0	0	0	1	0	0
0	0	1	0	0	0
0	0	1	1	0	0
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	1	1	0
1	0	0	0	0	1
1	0	0	1	0	1
1	0	1	0	1	0
1	0	1	1	0	0
1	1	0	0	0	0
1	1	0	1	0	1
1	1	1	0	1	1
1	1	1	1	1	0

$$S_1: A=B$$

$$A_1=B_1 \text{ et } A_0=B_0$$

$$S_2: A>B$$

$$A_1 > B_1 \text{ ou } (A_1=B_1 \text{ et } A_0 > B_0)$$

Inferieur:

$$A_1 < B_1 \text{ ou } (A_1=B_1 \text{ et } A_0 < B_0)$$

$$3) S_1 = \bar{A}_1 \bar{A}_0 \bar{B}_1 \bar{B}_0 + \bar{A}_1 A_0 \bar{B}_1 \bar{B}_0 + A_1 \bar{A}_0 B_1 \bar{B}_0 + A_1 A_0 B_1 B_0$$

$$S_2 = \bar{A}_1 A_0 \bar{B}_1 \bar{B}_0 + \bar{A}_1 \bar{A}_0 \bar{B}_1 \bar{B}_0 + \bar{A}_1 \bar{A}_0 B_1 \bar{B}_0 + A_1 A_0 \bar{B}_1 \bar{B}_0 + A_1 A_0 \bar{B}_1 B_0 + A_1 A_0 B_1 \bar{B}_0$$

4)


$$S_1 = \bar{A}_1 \bar{B}_1 (\bar{A}_0 \bar{B}_0 + A_0 B_0) + A_1 B_1 (A_0 B_0 + \bar{A}_0 \bar{B}_0) \\ = \bar{A}_1 \bar{B}_1 (\bar{A}_0 \oplus B_0) + A_1 B_1 (A_0 \oplus B_0) \\ = (A_0 \oplus B_0) (\bar{A}_1 \bar{B}_1 + A_1 B_1)$$

$$S_1 = (A_0 \oplus B_0) (A_1 \oplus B_1)$$


A ₁ A ₀ B ₁ B ₀	00	01	11	10
00	0	1	1	1
01	0	0	1	1
11	0	0	0	0
10	0	0	1	0

$$S_2 = \bar{A}_1 \bar{B}_0 + A_0 \bar{B}_0 \bar{B}_1 + A_1 A_0 B_1$$

5)

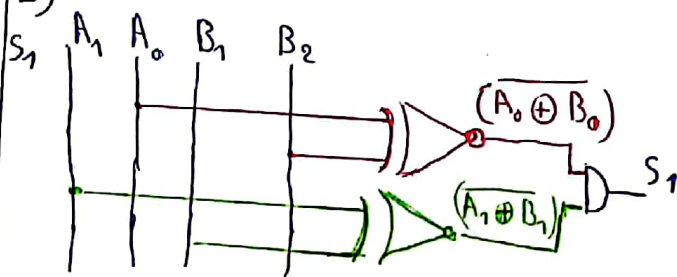


S₂

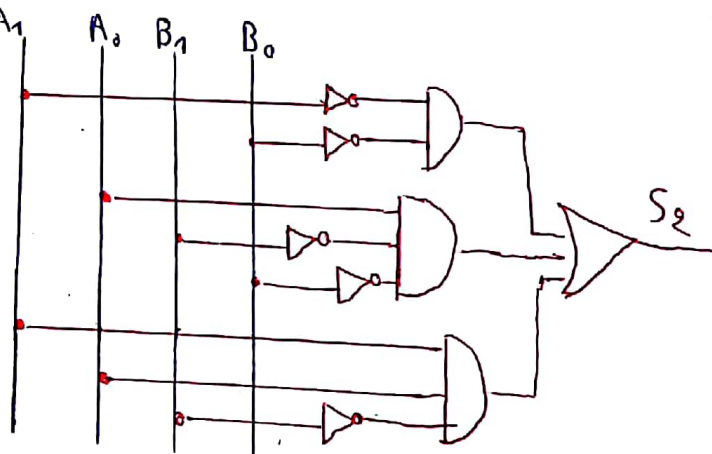

Exercise 2:

	A	B	C	D	u	v	w	x	y	z	t
0	0	0	0	0	1	1	1	1	1	0	1
1	0	0	0	1	1	1	0	0	0	0	0
2	0	0	1	0	1	0	1	1	0	1	1
3	0	0	1	1	1	1	1	0	0	1	1
4	0	1	0	0	1	1	0	0	1	1	0
5	0	1	0	1	0	1	0	1	1	1	1
6	0	1	1	0	0	1	1	1	1	1	1
7	0	1	1	1	1	1	0	0	0	0	1
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	1	1	1

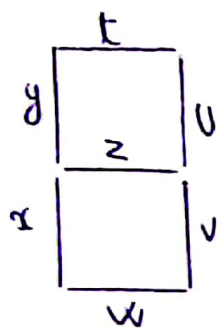

2)

u	AB \ CD	00	01	11	10
00	00	1	1	X	1
01	01	1	0	X	1
11	11	1	1	X	X
10	10	1	0	X	X

$$u = \bar{C}\bar{D} + CD + \bar{B}$$

$$= (\bar{C} \oplus D) + \bar{B}$$

v	AB \ CD	00	01	11	10
00	00	1	1	X	1
01	01	1	1	X	1
11	11	1	1	X	X
10	10	0	1	X	X

$$v = \bar{C} + D + B$$

w

w	AB \ CD	00	01	11	10
00	00	1	0	X	1
01	01	0	1	X	1
11	11	1	0	X	X
10	10	1	1	X	X

$$w = A + B\bar{C}D + C\bar{D} + C\bar{B} + \bar{B}\bar{D}$$

x

x	AB \ CD	00	01	11	10
00	00	1	0	X	1
01	01	0	0	X	0
11	11	0	0	X	X
10	10	1	1	X	X

$$x = C\bar{D} + \bar{B}\bar{D}$$

y

y	AB \ CD	00	01	11	10
00	00	1	X	X	1
01	01	0	1	X	1
11	11	0	0	X	X
10	10	0	1	X	X

$$y = \bar{C}\bar{D} + B\bar{C} + B\bar{D} + A$$

z

z	AB \ CD	00	01	11	10
00	00	0	1	X	1
01	01	0	1	X	1
11	11	1	0	X	X
10	10	1	1	X	X

$$z = B\bar{C} + C\bar{D} + \bar{B}C + A$$

$$= \bar{B} \oplus C + C\bar{D} + A$$

t

AB \ CD	00	01	11	10
00	1	0	X	1
01	0	1	X	1
11	1	1	X	X
10	1	1	X	X

$$t = A + C + DB + \bar{B}\bar{D}$$

$$= A + C + (\bar{B} \oplus \bar{D})$$

$$u = \bar{C} \oplus \bar{D} + \bar{B}$$

$$v = \bar{C} + D + B$$

$$w = A + B\bar{C}D + C\bar{D} + C\bar{B} + \bar{B}\bar{D}$$


$$= A + BCD + C\bar{D} + C\bar{B} = A + B\bar{C}D + C(\bar{D} + \bar{B})$$

$$x = C\bar{D} + \bar{B}\bar{D}$$

$$y = C\bar{D} + B\bar{C} + B\bar{D} + A = B(\bar{C} + \bar{D}) + A$$


$$z = (\bar{B} \oplus \bar{C}) + C\bar{D} + A$$

$$t = A + C + (\bar{B} \oplus \bar{D})$$

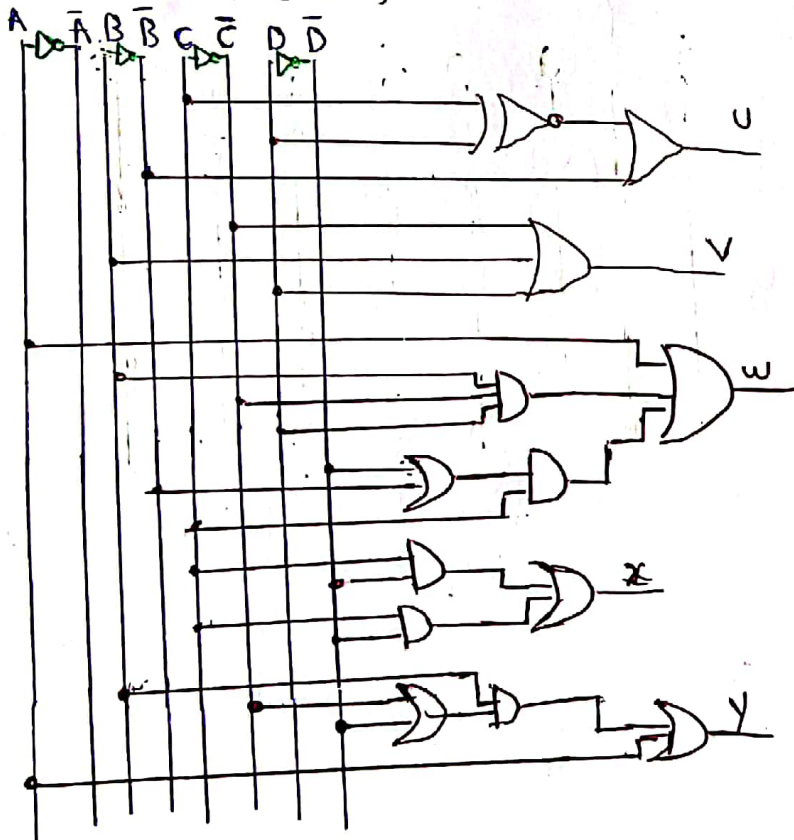

Exercice 3:

1)

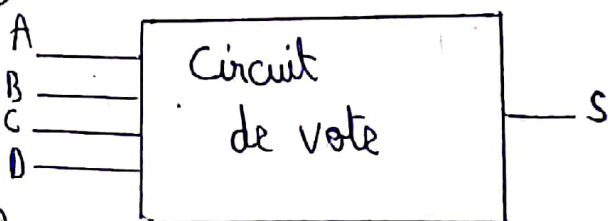

2)

A	B	C	D	S
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

⇒ à partir
nombre de votes

A=1 ⇒ 2 votes

B ou C ou D=1
= 1 vote

S < 2 votes = 0

S > 2 votes = 1


3)

AB \ CD	00	01	11	10
00	0	0	1	0
01	0	0	1	1
11	0	1	1	1
10	0	0	1	1

$$S = AB + AC + AD + BCD$$


4)

A B C D

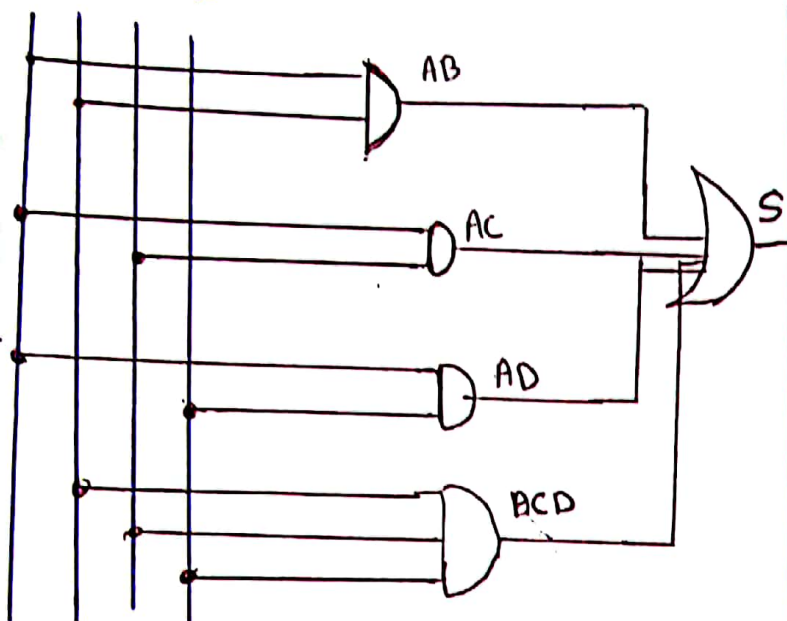

Exercice 4:


1)

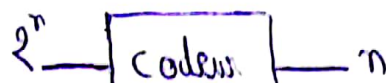

2) 16 bits d'entrée et 4 bits sorties

e_1	e_2	e_3	e_4	e_5	e_6	e_7	e_8	e_9	e_{10}	A	B	C	D
0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	0	0	0	1	0	0
0	0	0	0	0	1	0	0	0	0	0	1	0	1
0	0	0	0	0	0	1	0	0	0	0	1	1	0
0	0	0	0	0	0	0	1	0	0	0	1	1	1
0	0	0	0	0	0	0	0	1	0	1	0	0	0
0	0	0	0	0	0	0	0	0	1	1	0	0	1

5)

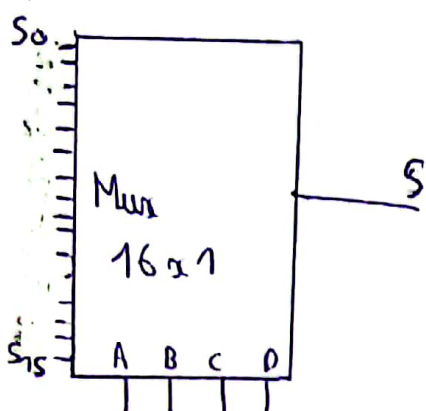

bits de selection

a) Multiplexeur 16x1

b) A: ligne selection

B, C, D: ligne d'activation

S_1, \dots, S_{15} : ligne d'entrée

S: sortie


$$S = \sum \{ S_7, S_9, S_{10}, S_{11}, S_{12}, S_{13}, S_{14}, S_{15} \}$$

$$A = e_3 + e_{10}$$

$$B = e_5 + e_6 + e_7 + e_8$$

$$C = e_3 + e_4 + e_7 + e_8$$

$$D = e_2 + e_4 + e_6 + e_8 + e_{10}$$

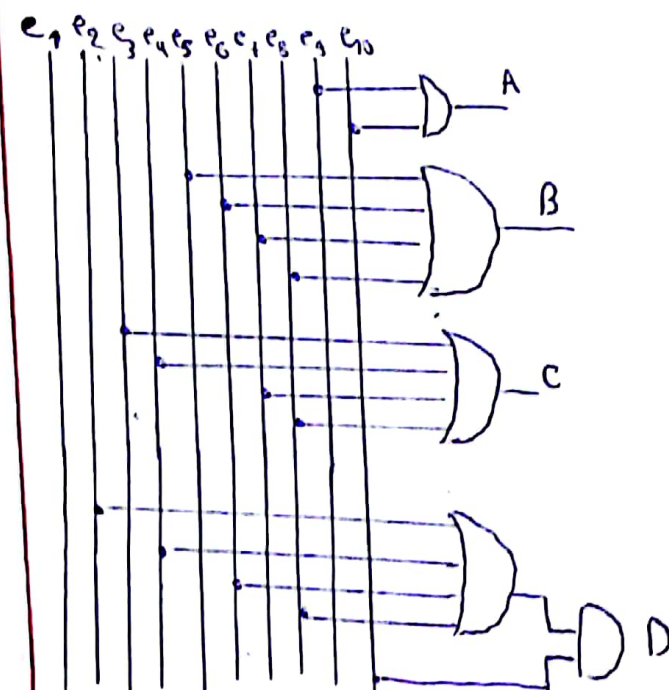

d)

	S_0	S_1	S_2	S_3	S_4	S_5	S_6	S_7
\bar{A}	S_0	S_1	S_2	S_3	S_4	S_5	S_6	S_7
A	S_8	S_9	S_{10}	S_{11}	S_{12}	S_{13}	S_{14}	S_{15}